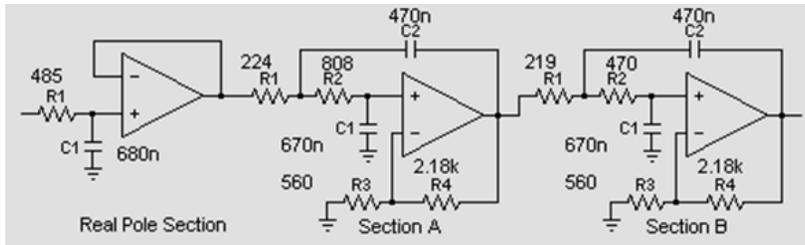


Active R/C Filter Design *and* 80M Unichip Plus DC XCVR



Dan Tayloe, N7VE
Ft. Tuthill, Az July 31, 2009



Topics

- R/C active filters
 - Use in receivers
 - Effect of Q on ringing
 - Effect of resistor values on noise
 - Distributed gain in multi-stage active R/C filters
- Three cw filters examples
 - Common parts values use
 - Minimum number of unique parts



Topics

- 80m Transceiver, Unichip “Plus”
 - Update of a simple VXO controlled, DC transceiver design
 - Uses R/C filters from above
 - Goals
 - Low cost, minimum number of unique parts
 - Good receiver audio filtering
 - Modern refresh to a classic design

Audio Filter Types

- L/C audio filters
 - Pro: Excellent for very low noise applications
 - Con: AC hum pick up + inductor cost
 - Con: Large and bulky or small and high loss
- SCAF (Switched Capacitor Audio Filter)
 - Pro: Compact, Cheap (\$1-\$2 ICs)
 - Pro: Sharp roll off, change cutoff frequency simply by changing clock frequency
 - Con: Noisy! Used at end of the audio chain
- R/C Active filters
 - Pro: Excellent for very low noise applications (receivers!)
 - Pro: Very large dynamic range (very small to very large signals)
 - Con: Relatively high parts count for good filters
 - Con: Tends to be fixed frequency cutoff

Dead simple SCAF circuit

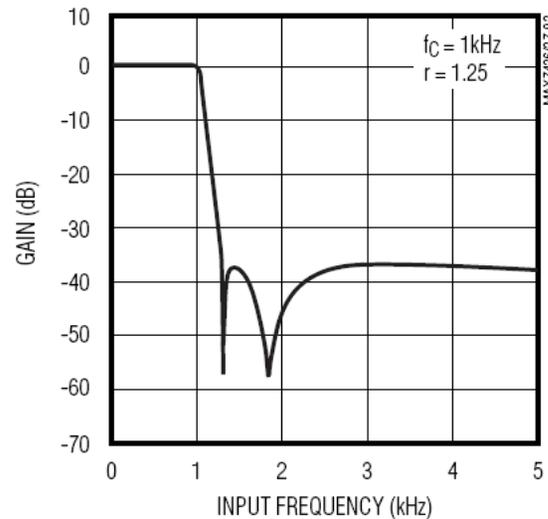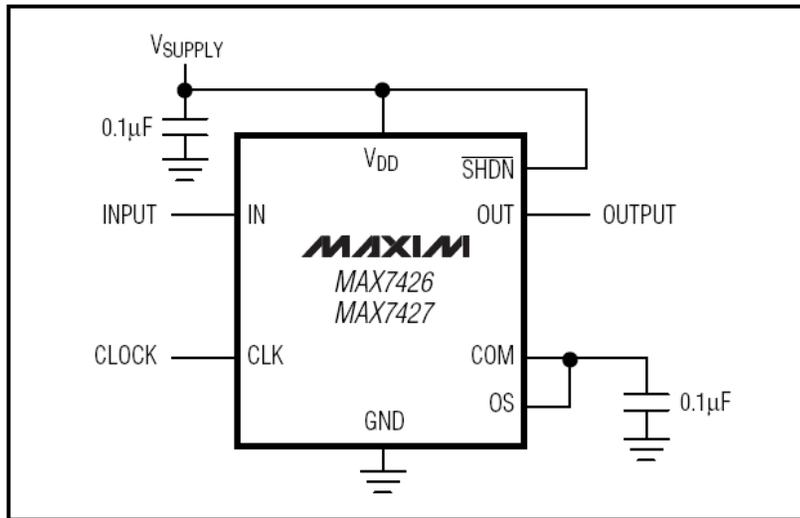

- Fixed frequency SCAF using a MAX7426 requires only a fixed cap on the “clock” ($\sim 180\text{ pf} = 1\text{ KHz}$)
- Simple, effective, sharp 40 dB cutoff
- Just need to AC couple inputs and outputs (0.1 uf)
- Need unity gain audio amp to drive headphones


Active R/C Design Topics

- Effect of Q on ringing
- Effect of resistor values on noise
- Distributed gain in multi-stage active R/C filters

Audio Filter Q Implications

- An R/C filter is (normally) composed of multiple one or two pole filter stages
- Each stage has a “Q”
- The higher the Q, the faster the steeper the frequency roll off
- Steeper frequency roll offs gets rid of QRM more quickly
- High Q in a filter is a good thing, right?

Audio Filter Q Implications

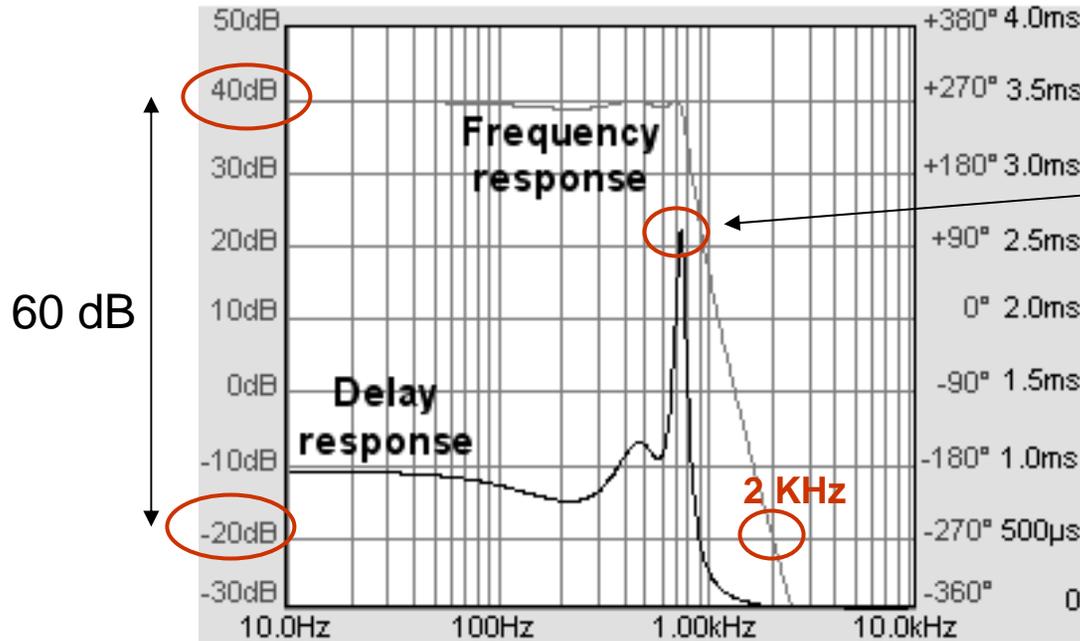


Note the very sharp delay spike at the cutoff frequency

Characteristic of high Q filters

Q = 5 here


- Example: 5th order Chebychev
 - 1 dB Ripple near cut off
 - 40 db total filter gain
 - 800 Hz cut off frequency
 - 60 dB of gain reduction at 2 KHz

High Q Problems

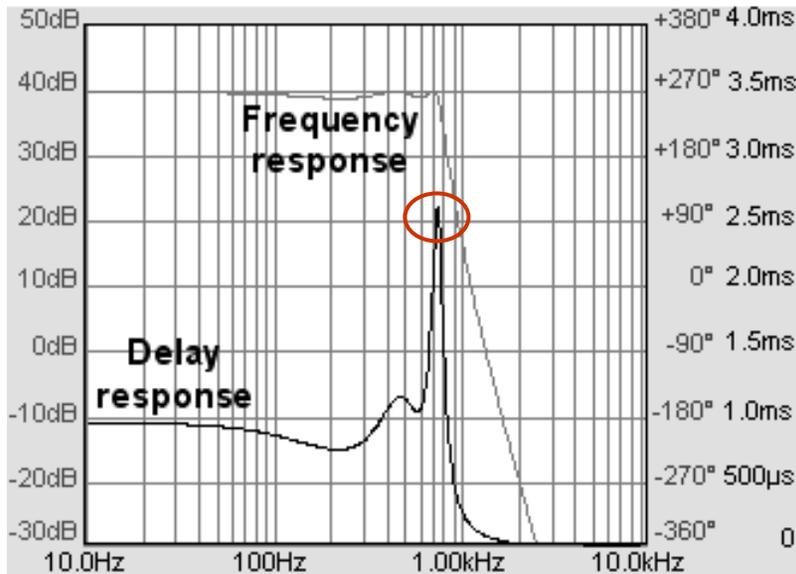


- High Q filters “ring” at the cut off frequency
 - *Very much like striking a bell*
 - Sharp blow to a bell causes it to ring
 - High Q filters are “*struck*” by *band noise* - *Ring*ing!
-
- Ringing typical of simple *cw crystal filters*
 - Bandpass response rings at both *high* & *low* edge
 - Can be very fatiguing to listen to when the band is noisy
 - Ears “don’t like” sharp delay/phase variations

Limit Use of Q

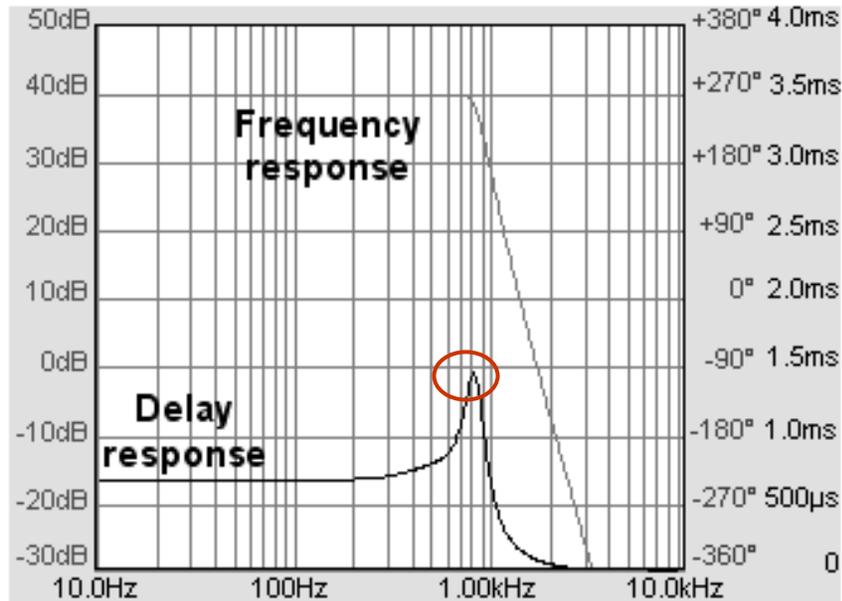

- Limiting Q to ~ 3 or less in R/C active filter sections minimizes the tendency to ring
 - Delay variations at filter edge are broader
 - Filter loses some roll off steepness
 - 48 db vs. 60 dB down at 2 KHz
- ⇒ However, filter sounds much better!*

Resistor Value Considerations

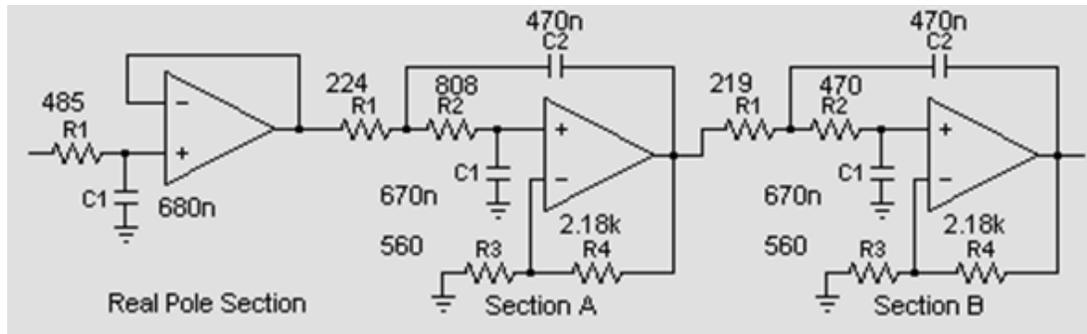


- *Resistors produce noise!*
 - 50 ohm resistor produces ~ 0.85 nV/SqrtHz
 - 4x the resistance produces 2x the noise voltage
 - 200 ohms produces ~ 1.75 nV/SqrtHz
 - 1M ohm => Squareroot(1000000/50)*0.85 = 120 nV/SqrtHz (*very high!*)
 - 10x voltage gain raises the noise floor, reduces the impact of resistor noise
 - 50 ohms of noise before 10x gain the same as a (10)*(10)*50 or 5K resistor after gain
 - Best audio op-amps produce 0.85 nV/SqrtHz, but are expensive (LT1115, \$4)
 - Cheap low noise op-amp (LM5532, LM833, \$0.30) produce ~4.5 nV/Sqrt Hz
 - Same noise as a (4.5/0.85)*(4.5/0.85)* 50 = 1400 ohm resistor
- => Use low value resistors (~200 to 500 ohms) in very low level audio work (like receiver front ends) before first filter gain stage


Filter Gain Considerations

- Almost all active R/C filters I have seen have *no* gain
- Receiver needs ~ *80 to 90 dB* of gain to drive headphones
- Volume control seems to work best placed at *mid point* in gain chain
 - Volume at the antenna or at the audio output causes problems
 - Halfway allows almost dead quite audio when the volume is turned all the way down
- Want ~ 40 dB of gain before volume control, 40 dB after
- If 40 dB gain *before* 1x gain filter, 40 dB gain section *overloads easily*
 - 40 dB section has no off frequency protection to strong signals
- If 1x gain filter is *first*, then 40 dB gain, *receiver is deaf*
 - Noise of op-amps and resistors in the 1x filter kills the sensitivity


Distributed Filter Gain – Powerful tool

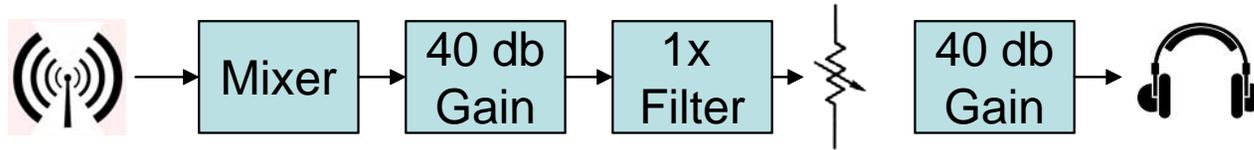

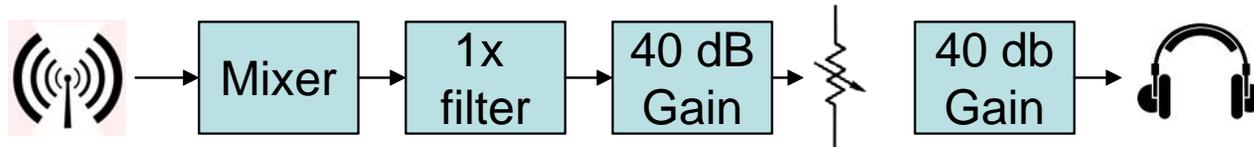- 40 dB gain block before filter subjected to *signal overload*




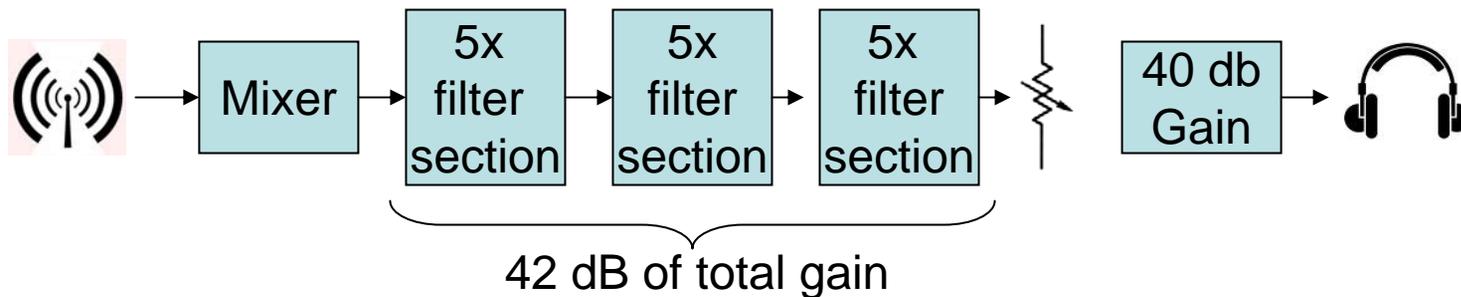- Too much filter noise at very weak signals – *deaf RX!*




- Best design: *Give each section of the filter a little bit of gain*
 - Normal filter has *multiple sections**=> Filter protected gain - Significantly higher RX performance*

Active R/C Filter Design Tool

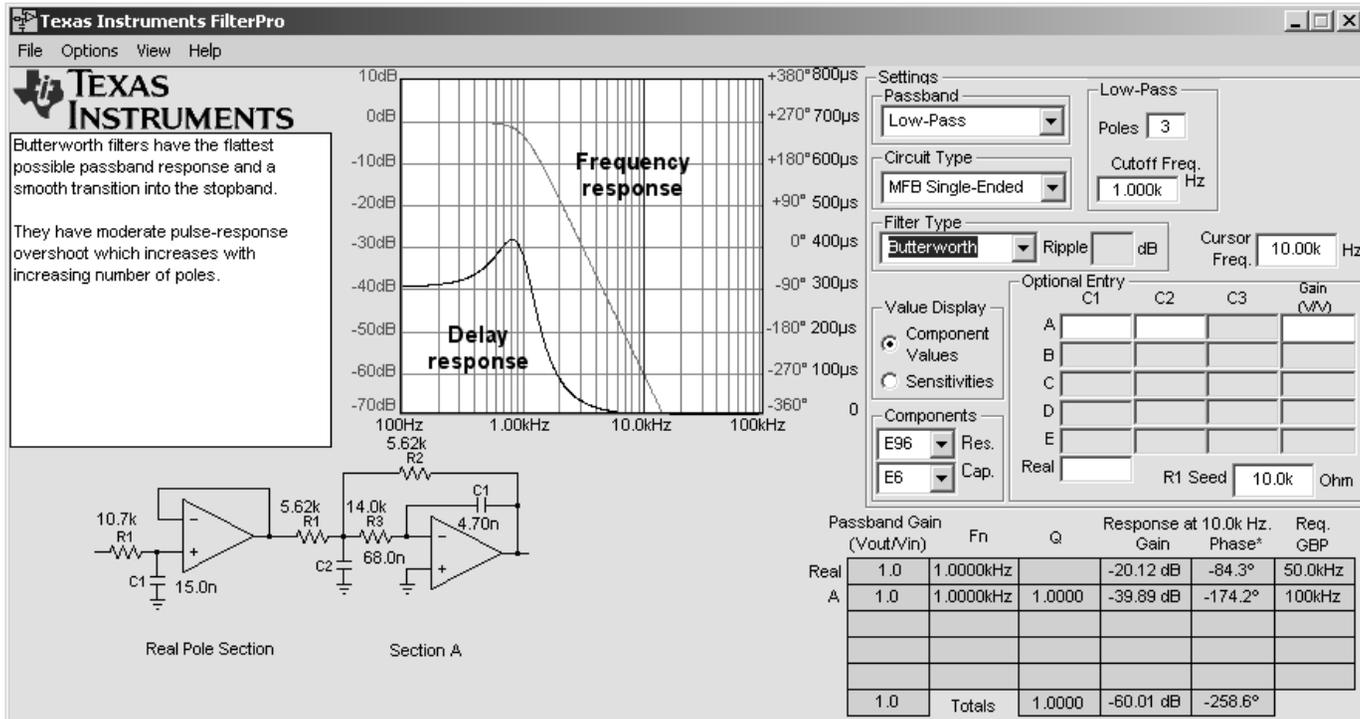


- TI FilterPro – Freeware available at <http://focus.ti.com/docs/toolsw/folders/print/filterpro.html>
 - or go to www.ti.com and search for “FilterPro”
- Designs Highpass, Lowpass or Band pass filters
 - Bandpass filters are simple low pass and high pass filters in series

Active R/C Filter Design Tool

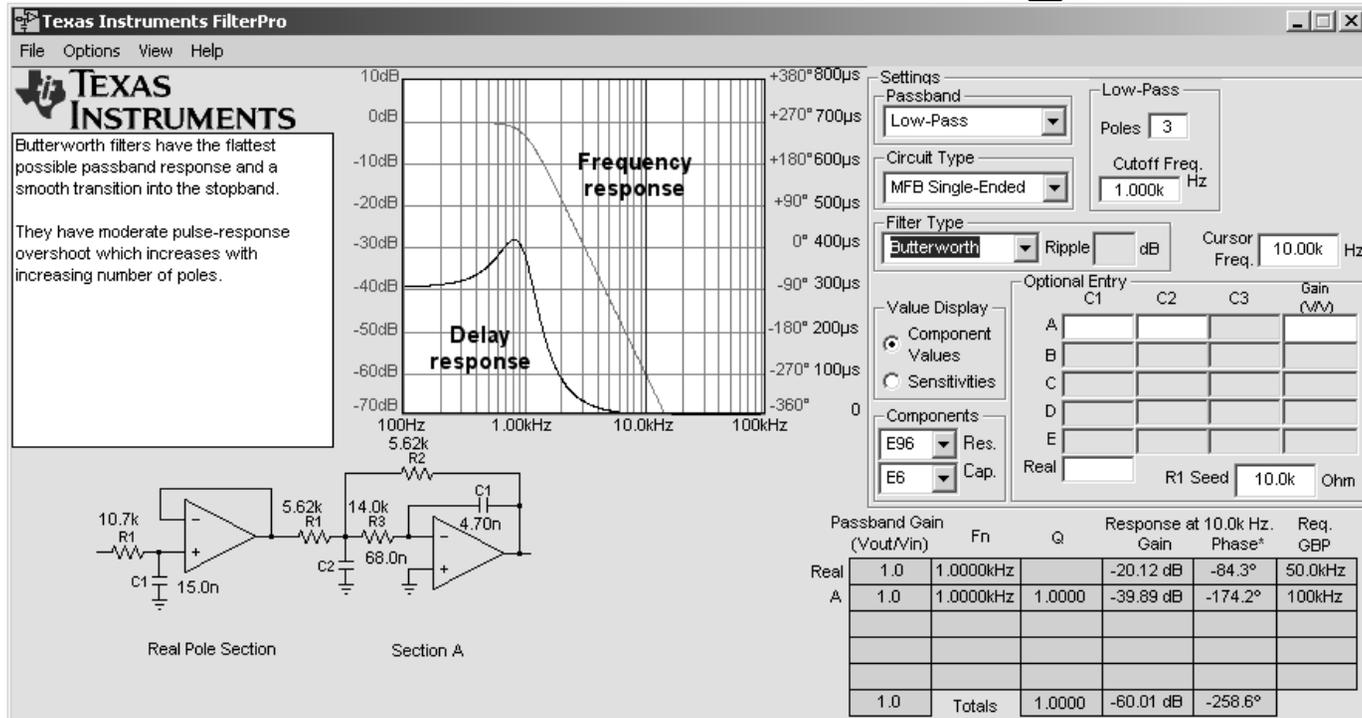


- Pick Chebychev filter
 - Changing Chebychev “ripple” changes the Q of the sections
 - *Allows designer to pick the maximum Q*
- Set the Circuit type from MFB to Sallen-Key
 - Gives better “C” values when used with gain
 - Set the R1 “seed” to 500 to 1K ohm (less noise)

Active R/C Filter Design Tool, cont

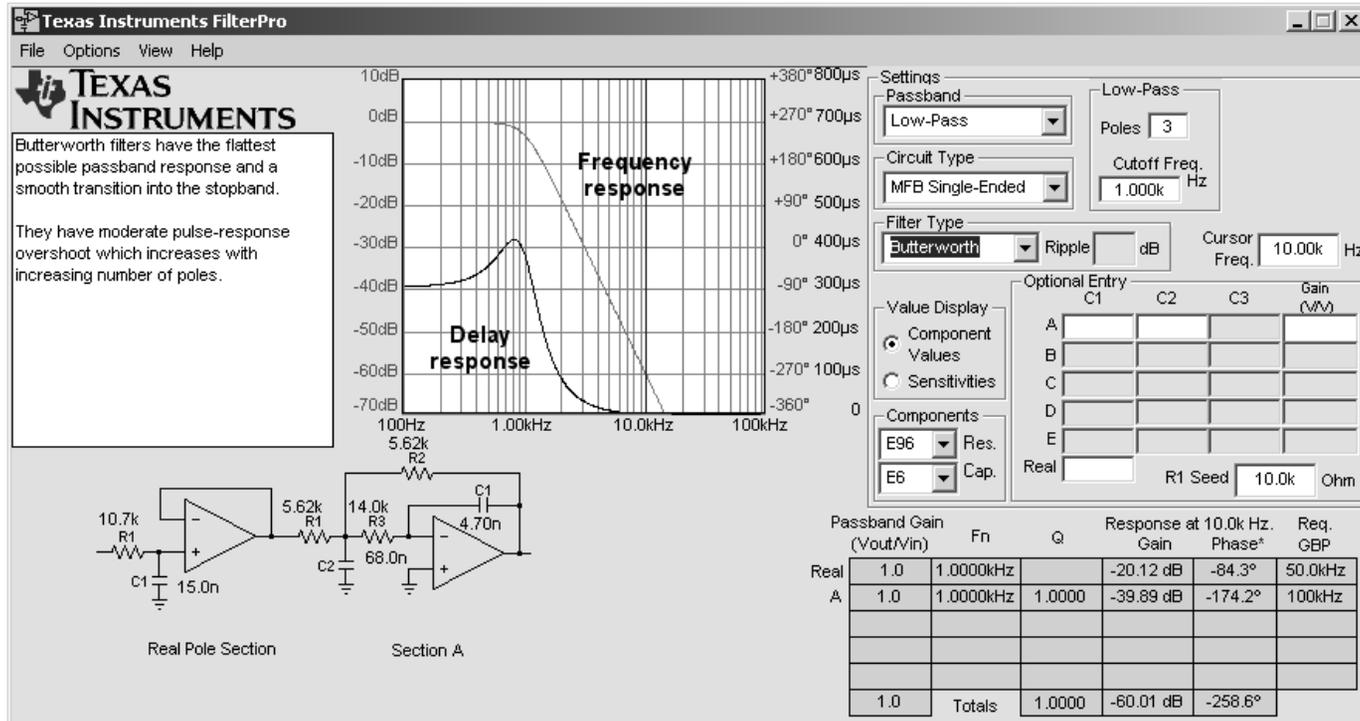


- Set cutoff frequency (800 Hz?)
- Adjust number of poles (3 used here) to get desired freq roll off speed
- Play with C1, C2 for each stage for best known resistor match
- Tweak “cutoff freq” and “ripple” to slightly adjust R values when close
- Goal: Get to as few unique parts as possible using common values

Sample CW Filters

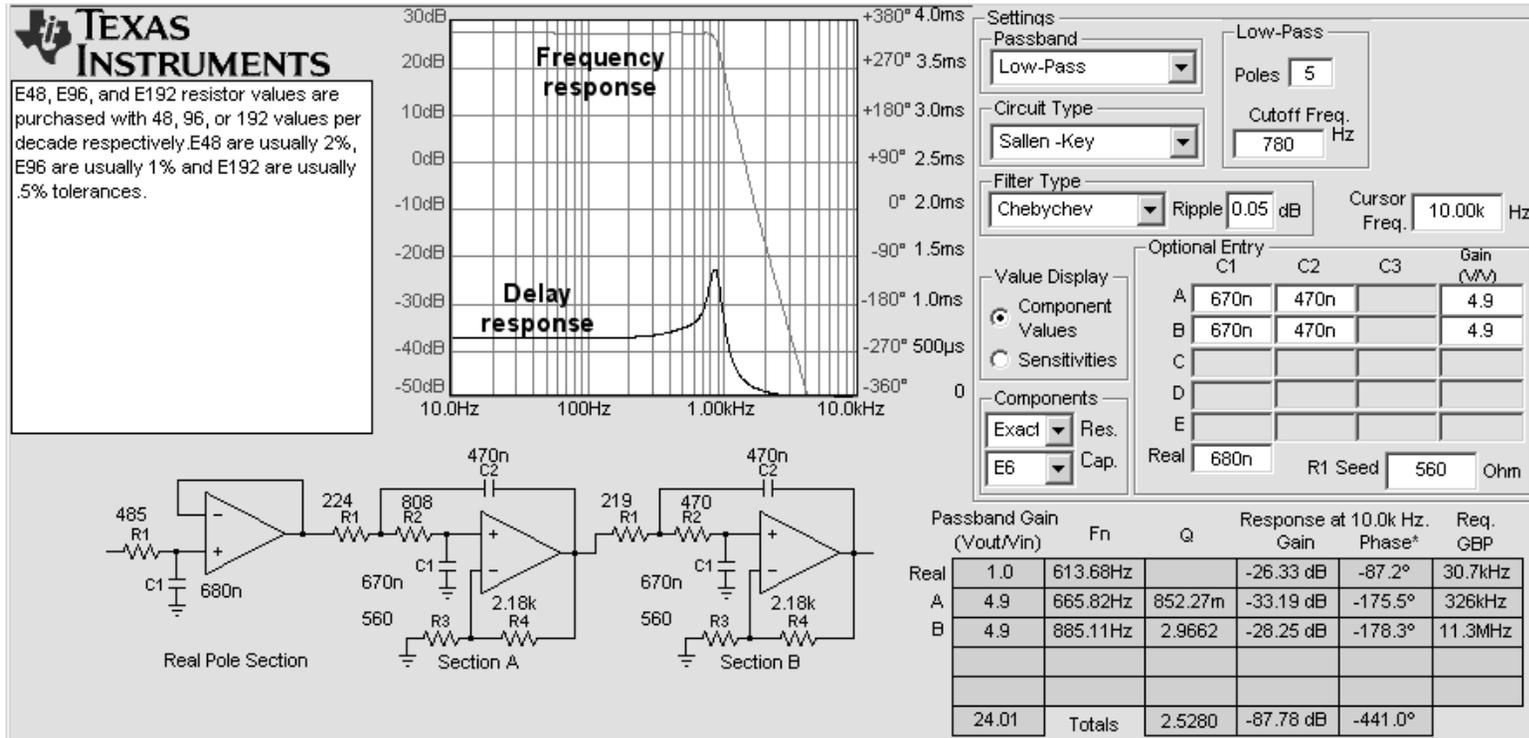


- Design # 1: 780 Hz, 48 dB down at 2 KHz
- Rs: 220, 470, 560, 2.2K (808 = 560 + 220)
- Cs: 0.47 uf, 0.1 uf (0.67 uf = 0.47uf + 2x 0.1uf)

Sample CW Filters

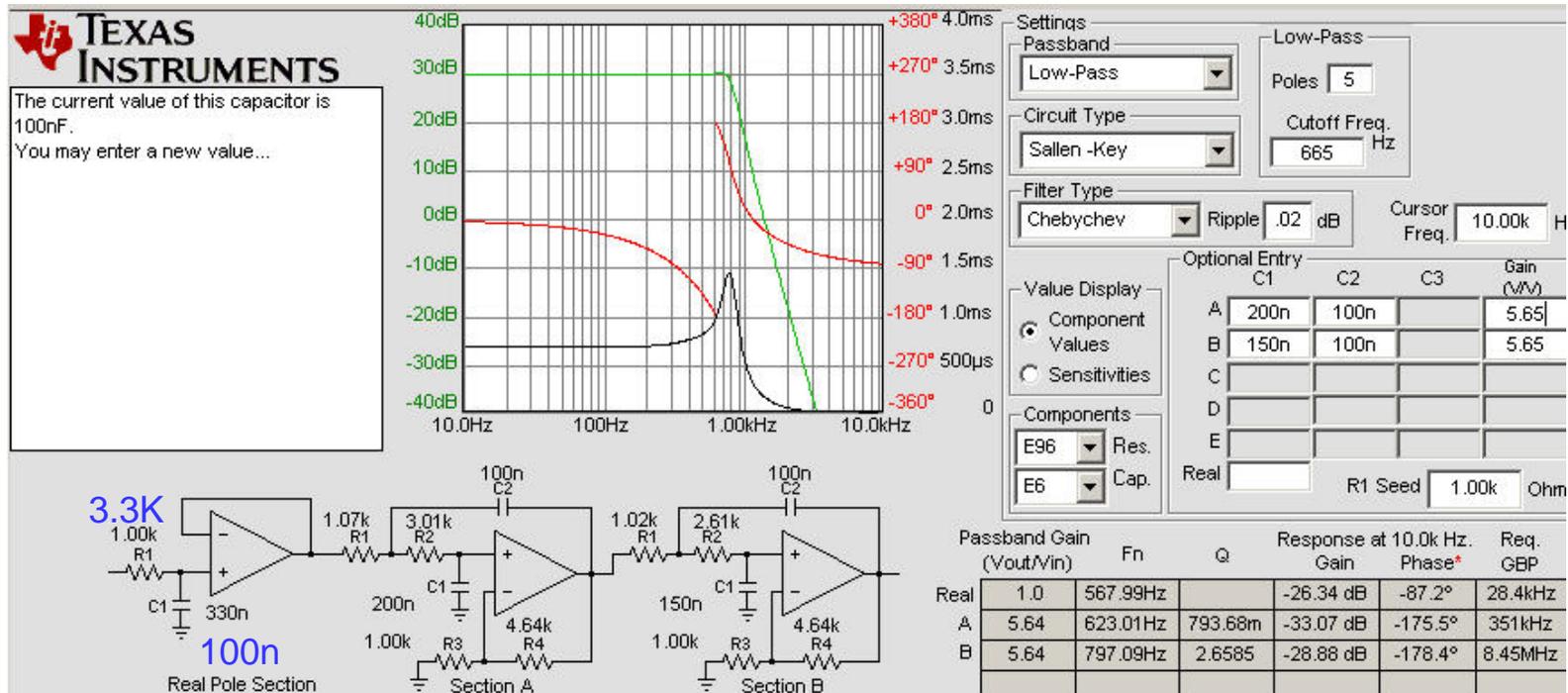

- Design # 2: 660 Hz, 50 dB down at 2 KHz
- Rs: 1K, 2.7K, 3.3K, 4.7K
- Cs: 0.1 uf (0.2 uf = 2x 0.1) (0.15uf = 0.1 + 2x 0.1 in series)
- 5 unique Rs and Cs total (out of 14 possible)

Sample CW Filters

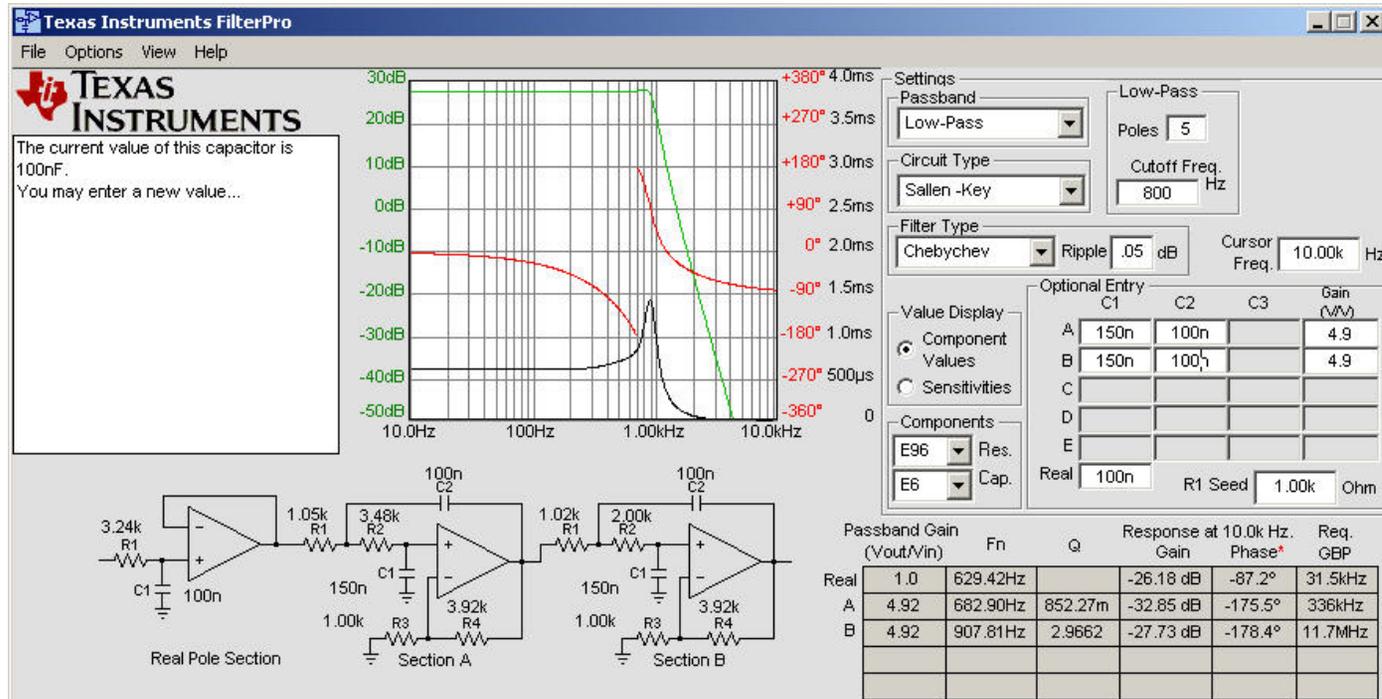


- Design # 3: 800 Hz, 46 dB down at 2 KHz
- Rs: 1K, 3.3K, 3.9K (2K = 2x 1K)
- Cs: 0.1 uf (0.15 uf = 0.1uf + 2x 0.1uf in series)
- Only 4 unique Rs and Cs total!

Main Take Away Points

- *Design tools* make R/C filter design easy
- Keep filter section Q *below ~3*
- *Beware of resistor noise!*
 - Use *low values* resistor for the first filter stage
 - 1M ohm resistors do not belong in very low level audio sections
- *Distributed gain* in each filter section produces high performance *filter protected* gain blocks
- Playing with the results can produce filters with both *few unique parts* and *common part values*

Original Unichip 80 DC Xcvr

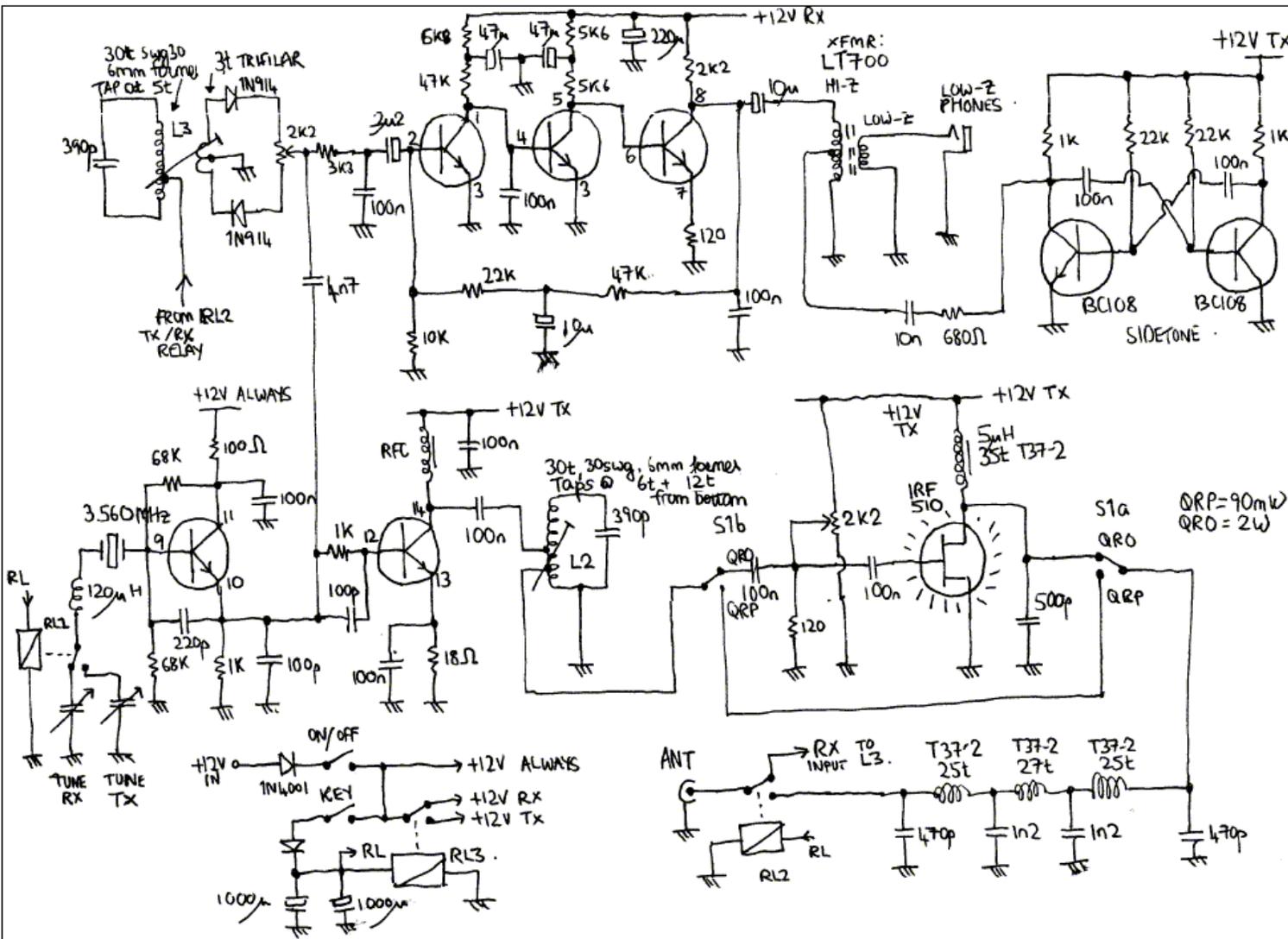


Observations

- 3 relays (\$1 to to \$2 each)
- \$2 Audio xfmr
- Slug tuned cores in RF tuned circuits
- No mute
- No volume control
- No TX Spot
- No key click filtering
- No RX-TX chirp protection
- No ear protection (audio limiter)

Aug 1, 2009

Unichip Plus Deadbug Prototype

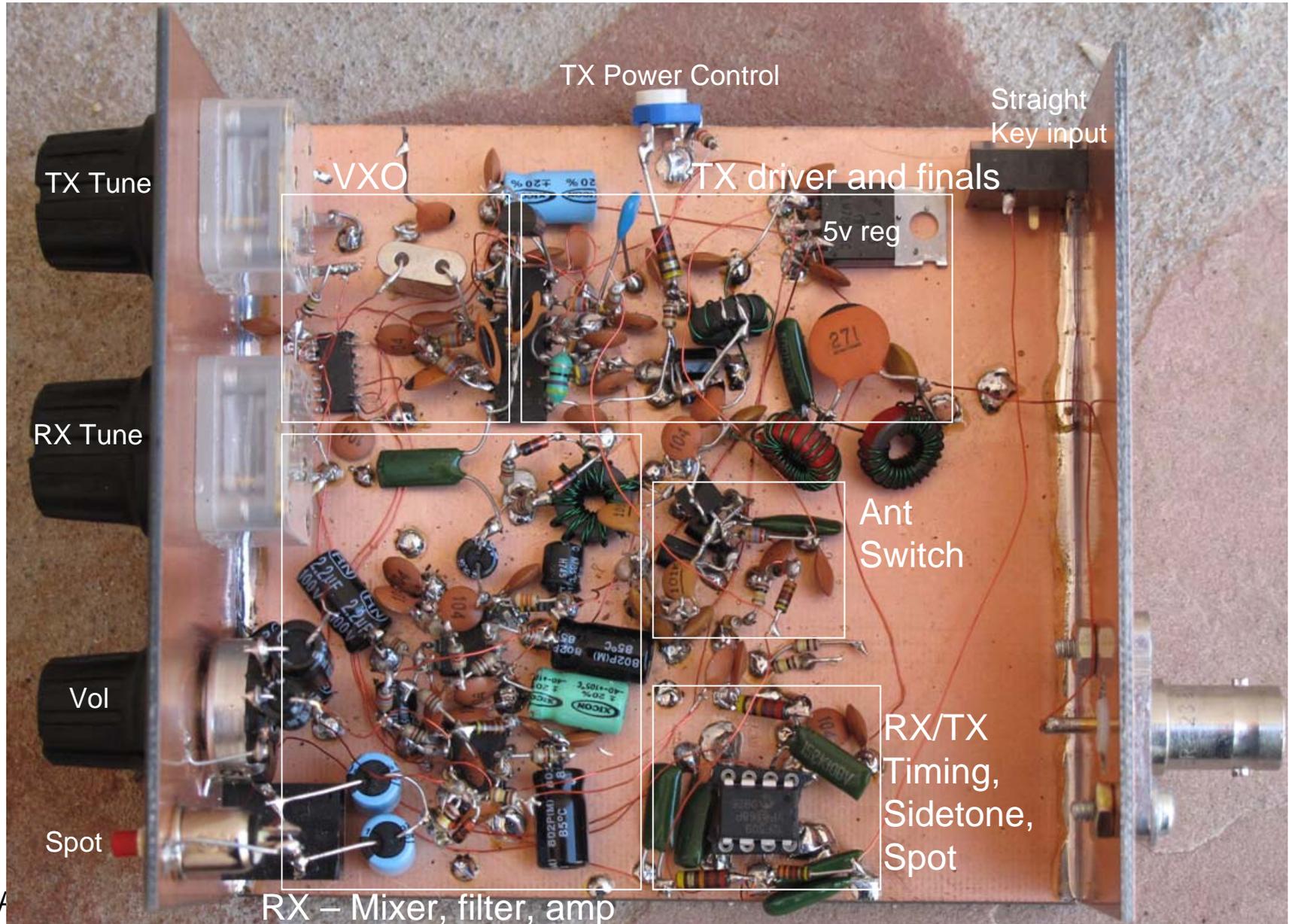

Unichip Plus 80m DC XCVR

- Three main goals in Unichip Plus Design
 - *Low total cost*
 - Low number of *unique parts*
 - Good RX audio filtering (*sharp + low noise + low distortion + no ring*)
 - Parts counts (excludes PCB, wire, and off board parts)
 - 2N2XX: 88 unique parts
 - BITX20: 57 unique parts
 - Unichip: 43 unique parts
 - DC40B: 38 unique parts
 - Unichip Plus: **28** unique parts, half are R's and Cs.
 - Unichip Plus uses only **6** R values, **7** C values
 - 47, 1K, 3.3K, 3.9K, 22K, 100K
 - 33 pf, 100 pf, 270 pf, 1000 pf, 0.1 uf, 2.2 uf, 33 uf
 - Some were combined (series/parallel) to make other values
- => *Fewer unique parts minimizes the kitting effort***



Unichip Plus Initial Specs

- Nominal Frequency: 3.5791 – 3.580 KHz
- VXO tuning range ~ 0.9 KHz (*not much!*)
- Current drain
 - RX: No signal 20 mA, moderate signal 23 mA
 - TX: 2-3w max. Output adjustable, 0.25w min, 680 mA @ 3.2w
- Receiver Sensitivity: -113 dBm (0.5 uV rms)
- Measured receiver filter response
 - 10 dB down at 1.4 KHz, 30 dB at 2 KHz
 - 50 dB down at 3 KHz, 70 dB at 4.8 KHz
 - 100 dB down at 9.4 KHz

Unichip Plus Improvements

- Mute circuit
- Volume control
- Sharper cw audio filter
- Diode protected audio output
- Spot switch
- Controlled RX-TX transition (no chirps, no key clicks)
- Low noise, low distortion audio chain
- “No Tune” RF filtering
- Improved DC power filtering
 - Eliminates DC receiver “howl”
- Improved VXO buffering
- No relays – solid state antenna switch

Unichip vs. Unichip Plus Freq Response

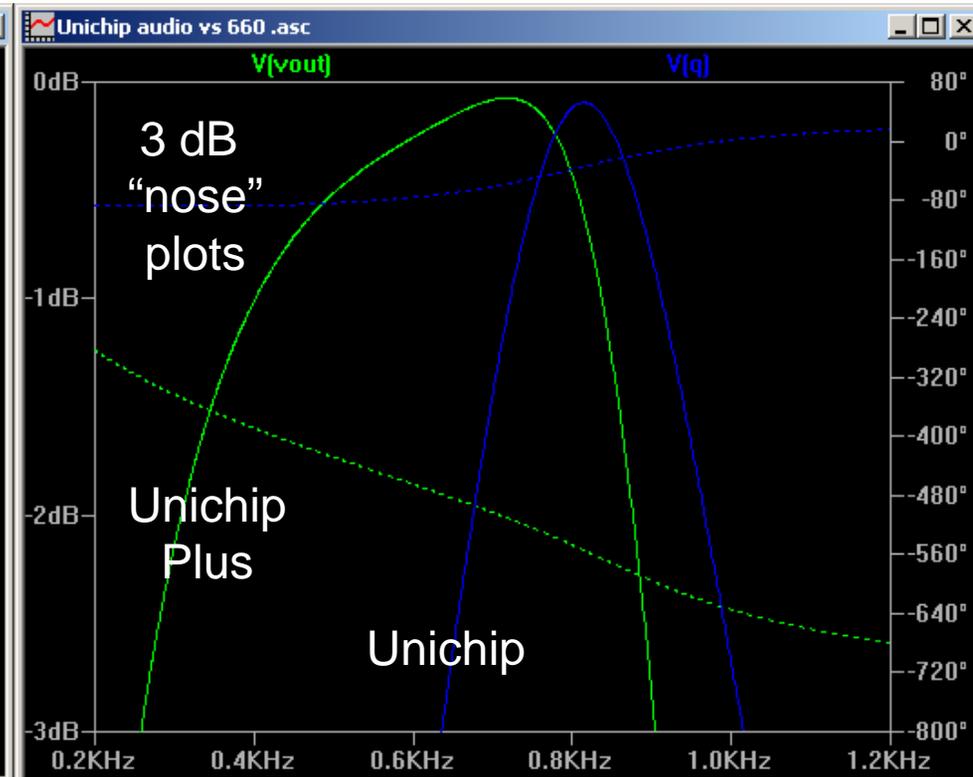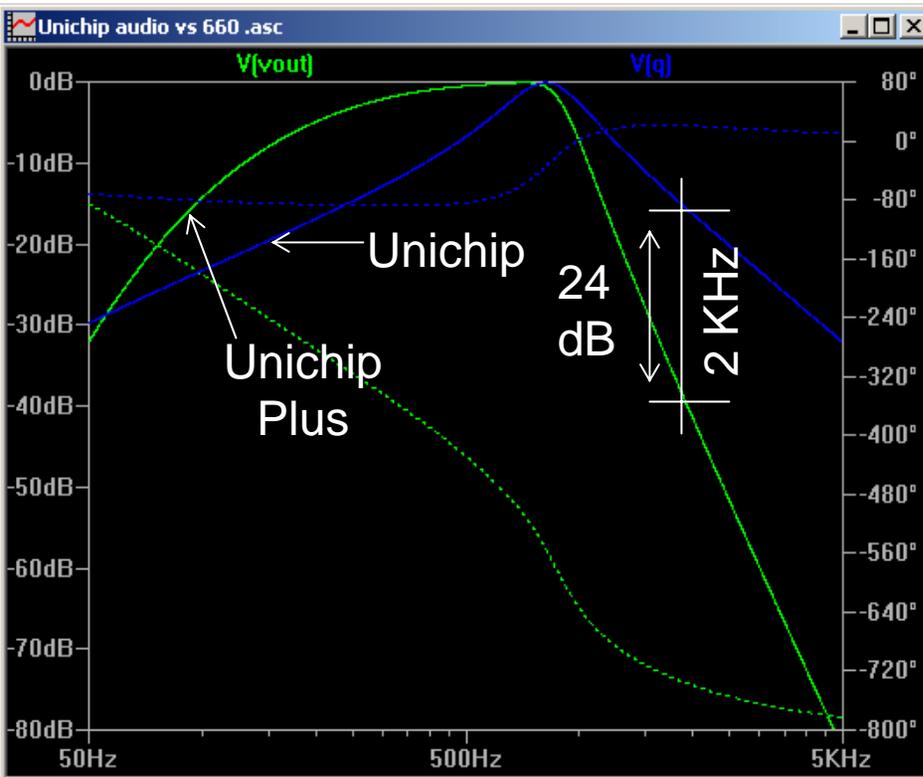

- Unichip Plus has wider 600 Hz audio pass band with much steeper high side filter cut off
 - 40 dB vs. 16 dB down at 2 KHz
 - 80 dB vs. 30 dB down at 5 KHz